

We will be generating a 5-to-32 decoder hierarchically in Verilog. Please begin by generating a 2-to-4 decoder defined as follows:

module decoder2_4(in[1:0], out[3:0])

Here's a basic implementation of a 2-to-4 decoder in Verilog:

```
module decoder2_4(  
    input [1:0] in,  
    output [3:0] out  
);  
  
    always @(in) begin  
        case (in)  
            2'b00: out = 4'b0001;  
            2'b01: out = 4'b0010;  
            2'b10: out = 4'b0100;  
            2'b11: out = 4'b1000;  
            default: out = 4'b0000;  
        endcase  
    end  
  
endmodule
```

Alternatively, you can use a more concise version using a combination of logic gates:

```
module decoder2_4(  
    input [1:0] in,  
    output [3:0] out  
);  
  
    assign out[0] = ~in[1] & ~in[0];  
    assign out[1] = ~in[1] & in[0];  
    assign out[2] = in[1] & ~in[0];  
    assign out[3] = in[1] & in[0];  
  
endmodule
```