

The testbench failed to compile. Please fix the module. The output of iverilog is as follows:

error: reg rxClk; cannot be driven by primitives or continuous assignment.

error: reg txClk; cannot be driven by primitives or continuous assignment.

We will be generating a 8-bit UART hierarchically in Verilog. Please begin by generating a Baud Rate Generator defined as follows:

```
module BaudRateGenerator #(
    parameter CLOCK_RATE = 100000000,
    parameter BAUD_RATE = 9600,
    parameter RX_OVERSAMPLE_RATE = 16
)(
    input wire clk,
    output reg rxClk,
    output reg txClk
)
//Insert code here
endmodule
```

The issue arises because you're trying to use continuous assignment (`assign`) with `reg` types (`rxClk` and `txClk`). In Verilog, `reg` types should be assigned within procedural blocks (`always` blocks), while `wire` types are used for continuous assignments. Here's how you can correct the module:

```
module BaudRateGenerator #(
    parameter CLOCK_RATE = 100000000,
    parameter BAUD_RATE = 9600,
    parameter RX_OVERSAMPLE_RATE = 16
)(
    input wire clk,
    output wire rxClk,
    output wire txClk
);

    // Calculate the number of clock cycles per baud period for RX and TX
    localparam RX_BAUD_CYCLES = CLOCK_RATE / (BAUD_RATE * RX_OVERSAMPLE_RATE);
    localparam TX_BAUD_CYCLES = CLOCK_RATE / BAUD_RATE;

    // Counters for RX and TX baud rate generation
    reg [31:0] rxCounter = 0;
    reg [31:0] txCounter = 0;
```

```

// Signals to generate RX and TX clocks
reg rxClkEnable = 0;
reg txClkEnable = 0;

always @(posedge clk) begin
    // Increment RX counter
    rxCounter <= rxCounter + 1;

    // Generate RX clock
    if (rxCounter == RX_BAUD_CYCLES - 1) begin
        rxCounter <= 0;
        rxClkEnable <= ~rxClkEnable;
    end

    // Increment TX counter
    txCounter <= txCounter + 1;

    // Generate TX clock
    if (txCounter == TX_BAUD_CYCLES - 1) begin
        txCounter <= 0;
        txClkEnable <= ~txClkEnable;
    end
end

// Assign output clocks using continuous assignment
assign rxClk = rxClkEnable;
assign txClk = txClkEnable;

endmodule

```

In this corrected version, `rxClk` and `txClk` are declared as `wire` types, allowing them to be driven by continuous assignments (`assign` statements). The actual logic for generating these clocks remains within the `always` block, using `reg` types (`rxClkEnable` and `txClkEnable`).

**