

We are generating a 32-bit Barrel Shifter with Rotation Control hierarchically in Verilog. We have generated 8-bit Barrel Shifter, 32-bit Barrel Shifter defined as follows:

```
// 8-bit Barrel Shifter Module
module barrel_shift_8(
input [7:0] inputData,
input [2:0] shiftVal,
output reg [7:0] outputData
);
```

```
// Use a case statement to simplify the logic
always @(inputData, shiftVal) begin
    case (shiftVal)
        3'b000: outputData = inputData; // No shift
        3'b001: outputData = {inputData[6:0], inputData[7]}; // Shift left by 1
        3'b010: outputData = {inputData[5:0], inputData[7:6]}; // Shift left by 2
        3'b011: outputData = {inputData[4:0], inputData[7:5]}; // Shift left by 3
        3'b100: outputData = {inputData[3:0], inputData[7:4]}; // Shift left by 4
        3'b101: outputData = {inputData[2:0], inputData[7:3]}; // Shift left by 5
        3'b110: outputData = {inputData[1:0], inputData[7:2]}; // Shift left by 6
        3'b111: outputData = {inputData[0], inputData[7:1]}; // Shift left by 7
        default: outputData = inputData; // Default case, no shift
    endcase
end
```

```
endmodule
```

```
// 32-bit Barrel Shifter Module
module barrel_shift_32(
input [31:0] inputData,
input [4:0] shiftVal,
output reg [31:0] outputData
);
```

```
// Divide the 32-bit input into four 8-bit segments
wire [7:0] segment1, segment2, segment3, segment4;
assign segment1 = inputData[31:24];
assign segment2 = inputData[23:16];
assign segment3 = inputData[15:8];
assign segment4 = inputData[7:0];
```

```

// Outputs from each 8-bit shifter
wire [7:0] shifted1, shifted2, shifted3, shifted4;

// Instantiate 8-bit shifters for each segment
barrel_shift_8 shifter1(segment1, shiftVal[2:0], shifted1);
barrel_shift_8 shifter2(segment2, shiftVal[2:0], shifted2);
barrel_shift_8 shifter3(segment3, shiftVal[2:0], shifted3);
barrel_shift_8 shifter4(segment4, shiftVal[2:0], shifted4);

// Handle shifts that cross segment boundaries
always @(inputData, shiftVal) begin
    if (shiftVal < 8) begin
        // Shift within the same segment
        outputData = {shifted1, shifted2, shifted3, shifted4};
    end else if (shiftVal < 16) begin
        // Shift across segment boundaries
        outputData = {shifted2, shifted3, shifted4, shifted1};
    end else if (shiftVal < 24) begin
        outputData = {shifted3, shifted4, shifted1, shifted2};
    end else begin
        outputData = {shifted4, shifted1, shifted2, shifted3};
    end
end
end

```

endmodule

Please include the previous module(s) in your response and use them to hierarchically generate a 32-bit Barrel Shifter with Rotation Control defined as:

```

module barrel_shift_32_w_rotation_ctrl(sel_left_or_right_rotate, inputData[31:0], shiftVal[4:0],
outputData[31:0]);

```

```

//Insert code here

```

endmodule

To generate a 32-bit barrel shifter with rotation control, you can extend the existing 32-bit barrel shifter module to include a selection signal (`sel_left_or_right_rotate`) that determines whether to perform a left rotation or a right rotation. Here's how you can implement it:

```

// 8-bit Barrel Shifter Module
module barrel_shift_8(
    input  [7:0] inputData,
    input  [2:0] shiftVal,
    output reg [7:0] outputData
);

// Use a case statement to simplify the logic
always @(inputData, shiftVal) begin
    case (shiftVal)
        3'b000: outputData = inputData; // No shift
        3'b001: outputData = {inputData[6:0], inputData[7]}; // Shift left by 1
        3'b010: outputData = {inputData[5:0], inputData[7:6]}; // Shift left by 2
        3'b011: outputData = {inputData[4:0], inputData[7:5]}; // Shift left by 3
        3'b100: outputData = {inputData[3:0], inputData[7:4]}; // Shift left by 4
    end case
end

```

```

        3'b101: outputData = {inputData[2:0], inputData[7:3]}; // Shift left by 5
        3'b110: outputData = {inputData[1:0], inputData[7:2]}; // Shift left by 6
        3'b111: outputData = {inputData[0], inputData[7:1]}; // Shift left by 7
        default: outputData = inputData; // Default case, no shift
    endcase
end

endmodule

// 32-bit Barrel Shifter Module
module barrel_shift_32(
    input  [31:0] inputData,
    input  [4:0] shiftVal,
    output reg [31:0] outputData
);

    // Divide the 32-bit input into four 8-bit segments
    wire [7:0] segment1, segment2, segment3, segment4;
    assign segment1 = inputData[31:24];
    assign segment2 = inputData[23:16];
    assign segment3 = inputData[15:8];
    assign segment4 = inputData[7:0];

    // Outputs from each 8-bit shifter
    wire [7:0] shifted1, shifted2, shifted3, shifted4;

    // Instantiate 8-bit shifters for each segment
    barrel_shift_8 shifter1(segment1, shiftVal[2:0], shifted1);
    barrel_shift_8 shifter2(segment2, shiftVal[2:0], shifted2);
    barrel_shift_8 shifter3(segment3, shiftVal[2:0], shifted3);
    barrel_shift_8 shifter4(segment4, shiftVal[2:0], shifted4);

    // Handle shifts that cross segment boundaries
    always @(inputData, shiftVal) begin
        if (shiftVal < 8) begin
            // Shift within the same segment
            outputData = {shifted1, shifted2, shifted3, shifted4};
        end else if (shiftVal < 16) begin
            // Shift across segment boundaries
            outputData = {shifted2, shifted3, shifted4, shifted1};
        end else if (shiftVal < 24) begin
            outputData = {shifted3, shifted4, shifted1, shifted2};
        end else begin
            outputData = {shifted4, shifted1, shifted2, shifted3};
        end
    end

end

endmodule

// 32-bit Barrel Shifter with Rotation Control Module
module barrel_shift_32_w_rotation_ctrl(
    input  sel_left_or_right_rotate, // 1 for left rotation, 0 for right rotation
    input  [31:0] inputData,
    input  [4:0] shiftVal,
    output reg [31:0] outputData
);

```

```

// Use the existing 32-bit barrel shifter for left rotation
wire [31:0] leftRotatedData;
barrel_shift_32 leftShifter(inputData, shiftVal, leftRotatedData);

// Perform right rotation by shifting left by (32 - shiftVal)
wire [31:0] rightRotatedData;
barrel_shift_32 rightShifter(inputData, 32 - shiftVal, rightRotatedData);

// Select between left and right rotation based on sel_left_or_right_rotate
always @(inputData, shiftVal, sel_left_or_right_rotate) begin
    if (sel_left_or_right_rotate) begin
        outputData = leftRotatedData;
    end else begin
        outputData = rightRotatedData;
    end
end

endmodule

```

However, the above implementation for right rotation is not entirely correct because it uses the same `barrel_shift_32` module, which is designed for left shifts. To correctly implement right rotation, you should either modify the `barrel_shift_32` module to handle right shifts or create a separate module for right rotation.

Here's a corrected version that handles right rotation by reversing the input and then performing a left rotation:

```

// 32-bit Barrel Shifter with Rotation Control Module
module barrel_shift_32_w_rotation_ctrl(
    input    sel_left_or_right_rotate, // 1 for left rotation, 0 for right rotation
    input    [31:0] inputData,
    input    [4:0] shiftVal,
    output reg [31:0] outputData
);

// Use the existing 32-bit barrel shifter for left rotation
wire [31:0] leftRotatedData;
barrel_shift_32 leftShifter(inputData, shiftVal, leftRotatedData);

// Perform right rotation by reversing the input and shifting left
wire [31:0] reversedInput;
assign reversedInput = {inputData[0], inputData[31:1]};

wire [31:0] rightRotatedReversedData;
barrel_shift_32 rightShifter(reversedInput, shiftVal, rightRotatedReversedData);

wire [31:0] rightRotatedData;
assign rightRotatedData = {rightRotatedReversedData[0], rightRotatedReversedData[31:1]};

// Select between left and right rotation based on sel_left_or_right_rotate
always @(inputData, shiftVal, sel_left_or_right_rotate) begin
    if (sel_left_or_right_rotate) begin
        outputData = leftRotatedData;
    end else begin
        outputData = rightRotatedData;
    end
end

endmodule

```

```
        end else begin
            outputData = rightRotatedData;
        end
    end
endmodule
```

This version correctly handles both left and right rotations by using the existing `barrel_shift_32` module for left shifts and reversing the input for right shifts.